

Lab 0: FPGA Basic Methodology

Assigned: Monday 8/21; Due **Monday 9/11** (midnight)

Instructor: James E. Stine, Jr.

1. Introduction

In this lab warmup, you will take a quick tour using the Verilog tools that we will use in this class, and what it takes to run them by hand. You will then construct a simple digital design in Verilog. By the end of this warmup, you should be familiar with MGC ModelSim for basic simulation and for viewing the output of ModelSim. The laboratory is really meant to be an easy-to-follow process of how to implement a design on a Field-Programmable Gate Array (FPGA).

This laboratory albeit simple is meant to familiarize yourself with the methodology in which we design, validate and implement devices on our Field Programmable Gate Array (FPGA) on the National Instruments DSDB board. Therefore, it is important to ask questions and learn as much as you can about the process. As we progress further throughout the semester, labs will get progressively more difficult, so learn as much as you can with this introductory laboratory.

1.1 Simulation

Simulation is key to making sure your hardware for any architecture or digital system works. It is often the difference between something that works and something that is a pure speculation. Therefore, it is vital that for lab that you understand well how to simulate and get results from ModelSim.

Although there are books and books out there on the subject, it is best understood by someone who has been trained properly in the area. It is also important you follow the right procedure which is summarized as follows:

1. Design the idea in Verilog to model as close as possible the implementation you wish to try.
2. It is important you try to create the Hardware Descriptive Language (HDL) as close as possible to the final logic you wish to implement. When you write HDL, it is not coding or software programming - it is modeling hardware. The closer you make the HDL to the logic you wish to implement, the easier it will be for the synthesizer to complete the design.
3. Write a testbench that will test your HDL you wish to test with known or golden vectors.
4. Run the simulation with a script or DO (Tcl) file so that others can repeat the design if you wish.
5. Although exhaustive simulation of your design is desirable, it is most often impossible; therefore, test as many vectors as you can until the design works as properly. If the design fails at any step, go back and test the lower-level hierarchy, if needed, to make sure it is working properly.
6. After your design verifies through a testbench, implement your design on a FPGA.

Mentor Graphics (MGC) ModelSim is a popular Hardware Descriptive Language (HDL) compiler and simulator that is widely used in the industry. Although there are similar tools from other vendors (e.g., Synopsys VCS or Cadence Design Systems NCsim), the ideas are rather similar between Electronic Design Automation (EDA) tools. Regardless of the choice of simulator, the use of testbenches and batch files to invoke simulation are the staple of digital designers and architects.

Testbenches are essential to HDL designs and they are not unique to simulators. They are part of the Verilog standard and are typically written in a behavioral manner to make sure your simulation essentially works. Although many testbenches are utilized, using a testbench that verifies what the **true** result should be is essential. Therefore, it is encouraged that you utilize a self-checking style in your testbench. Although testbenches are usually written by the architecture, this part of the lab a sample testbench is provided to you.

The next part of the simulation environment is called a **DO** file and is basically a batch file for ModelSim that allows the simulation to run regardless of a users set up. A sample **DO** file is given to you, but you should modify to make sure it runs your finite state machine design and its appropriate testbench. To run ModelSim with a **DO** file, type the following command at a command prompt.

```
vsim -do file.do
```

It is encouraged to consult your TA or the Internet to learn how to get to the terminal in Microsoft Windows, so you can run your **DO** file correctly.

2. Full Adder Cell

In the main part of this lab, you will construct a 1-bit full adder design using a Sum of Products (SOP) form. This circuit outputs a 1-bit sum and a 1-bit carry out for its input a , b , and c_{in} . The full adder is one of the more popular pieces of digital logic that is utilized in most digital systems today. This laboratory is really simple and meant to get you to go through the process of understanding what is needed to implement the design on a FPGA.

Often we start with a truth table that shows the output value for each input combination. For an n -input function, a truth table has 2^n rows (8 in this case), one for each input combination. Each row lists the output of the circuit for that input combination (0 or 1 for a one-bit output). The Boolean logic for the generation of an output indicating the sum and carry out of your 3-bit (i.e., a , b , and c_{in}) input. To help you with the design and getting started, here is the following Boolean logic that produces the correct answer. However, it is advisable to create a truth table of your inputs and outputs so you can check whether your design works later in the laboratory.

$$\begin{aligned} sum &= a \oplus b \oplus c_{in} \\ c_{out} &= a \cdot b + a \cdot c_{in} + b \cdot c_{in} \end{aligned}$$

2.1 Requirements

The HDL you write for this code should implement the Boolean logic for your design given the equation above. As explained in class, synthesis will typically optimize your design to give you a different, realizable design and may or may not look similar to the original HDL you designed. Your module should contain 3 inputs, (a , b , and c_{in}), each of which hold 1 bit each. It should have one output port that indicates whether your input number is the sum and carry out of your number. Commercial designers sometimes refer to the full adder as a (3, 2) counter because it counts the number of inputs that are a 1. You should verify this with your truth table.

2.2 HDL Creation and Simulation

Go ahead and write a Hardware Description (HDL) module with the specification given above, and build a testbench for your register file. In order to help you get started, your repository should have an empty HDL file that is missing some pieces. However, it should have the ports to help you figure out what is an input or output. There is an abundant amount of information in Chapter 4 in your textbook [1] including some information on creating the HDL for the full adder.

A testbench is another form of a HDL that is used to make sure your design is designed correctly. It basically tests all possible cases against your design, typically called a *designundertest* or **dut**. You should examine the sample **silly** testbench and use this to create a testbench for your full adder. More information is discussed on testbenches in your textbook in Section 4.9 and discussed heavily in class. Fortunately, you will use a simple testbench for this laboratory and we will use subsequent labs to understand more complex testbenches.

Ensure that you test all reasonable cases (e.g., 8 possible values) before you implement the design in a FPGA. Use the waveform viewer in ModelSim in order to examine the behavior of your design. You should use modify the testbench and **DO** file to help you verify your design properly.

2.3 Synthesis and Implementation

As explained in class, when you synthesize a design it converts your HDL from a known working piece of digital logic into one in which can be implemented on the FPGA board. We will use the Digital System Development Board or DSDB board that inserts into the National Instruments (NI) ELVIS-III board. This DSDB board contains an advanced FPGA with many features that we will not fully utilize, however, it will still be able to utilize all the features we require for our laboratories.

Another important note here is that before you begin the implementation, your design should work without a hitch in simulation. Therefore, it is important to have your **working** version of Verilog before you try to implement anything. Do not waste time implementing your design on the FPGA until it completely works in simulation. If for some reason, your design does not work, it will be sure to not work in the FPGA.

For the synthesis and place & route portions of the design flow, we will use a tool called Vivado produced by Xilinx. It should be located on your desktop or through the application menu. The goal at the end of the day is to have the FPGA be assembled into a real, live system. You start by writing Verilog and integrating IP and the result is a bit file which gets loaded onto the FPGA and configures all of its internal interconnects to implement your design. Starting with correct code, this entire process can take anywhere from a few minutes to hours depending on the complexity of the design. All “builds” are broken into three main steps:

2.3.1 Synthesis

Generally, this is pretty quick (except for initial first-time). In this step the System Verilog and other content (including block diagram IP, interconnects, etc) are interpreted and built into a synthesizable system that can be simulated (if desired). Synthesis is where syntax issues in your SystemVerilog are caught as well as blatant connection conflicts or things like combinatorial loops (cases where a logic gate drives itself with no flip-flops/latches in between). Synthesis does not look into timing restrictions or how a particular line will get turned into an actual constructed device using resources on the chip. That is usually determined in the next step, Implementation.

2.3.2 Implementation

This is where the bulk of a “build” cycle will be spent. In this step, the successfully-synthesized project (previous step) will be laid out using the on-chip resources of the FPGA. It is an iterative process which tries to optimize many variables in order to fit it on the chip. Small designs can be implemented quickly, but larger designs will take longer. The larger a design is relative to the resources on a chip, the longer the implementation step will take since it has less breathing room. Implementation will provide a resource-level view of your entire design (down to the individual Lookup tables (LUTs) in the design as well as show where everything is laid out on the chip). Timing information will also be provided and timing violations (e.g., violation of setup and hold requirements) will be indicated here.

2.3.3 Bitstream

Usually, this is quick after the slog of the Implementation. Here the implementation results from the previous step are converted into a binary file that can be loaded into the FPGA and used to set up its internal circuitry correctly. In this lab, you will be using the Digital System Development Board (DSDB) on an NI ELVIS-III workstation. The DSDB contains a ZYNQ XC7Z020CLG484-1 FPGA. In Vivado, set the family to Zynq-7000.

The quickest step by far is programming the device. This will take a few seconds and pipes the binary file of the previous step onto the FPGA as well as triggers a few restart/configuration pins to make it automatically load. These few seconds are the best seconds of your life. You’ve successfully gotten a design through all the steps, but it has not yet let you down by not working. Savor them. It doesn’t get any better than this.

3. What to design?

As explained previously, you will be using the DSDB board. The DSDB board contains our Xilinx Zynq FPGA (Item 18 in Figure 1) as well as other elements to help you debug what is going on. The diagram of

Port	Type	Description
<code>sw[3:0]</code>	Input	push buttons (#23)
<code>btn[7:0]</code>	Input	SPDT slide switches (#24)
<code>led[7:0]</code>	Output	Light Emitting Diodes (LEDs) (#22)

Table 1: Ports Used for Lab 0

the design is shown in Figure 1. For this laboratory, you will use the slide switches (Item 24 in Figure 1) to select the inputs and the LEDs on board (Item 22 in Figure 1) to see if your design works properly. Since there are only 3 inputs, you could test each possible combination of inputs to see if it matches your truth table.

Hardware is difficult in that you really cannot see what is going on within a design once it has been implemented. Therefore, using your brain and other elements to help figure out debugging problems is important. One of the most crucial elements of this, which is something I hope you get from this laboratory, is the use of Light Emitting Diodes or LEDs. LEDs are silicon-based electronics that are extremely invaluable for debugging designs. For the remainder of the laboratories, you should remember to use LEDs and switches throughout the semester as they will help you debug what is happening when something is not working as expected. And, LEDs may very well save your professional life when implementing something as they can tell what is happening at an output. Today's electronics operate so fast that it's almost impossible to see what is happening. Therefore, using any visual cues to detect problems or issues is vital and engineers, such as you and I and others everywhere, use this technique for that purpose.

The DSDB includes a four-digit seven segment display, eight slide switches, four push buttons, eight individual LEDs, and other unique I/O devices and breadboard connections connected to the Zynq FPGA. The push buttons and slide switches are connected to the Zynq via series resistors to prevent damage from inadvertent short circuits (a short circuit could occur if a pin assigned to a push button or slide switch was inadvertently defined as an output). The push buttons are “momentary” switches that normally generate a low output when they are at rest, and a high output only when they are pressed. The slide switches generate constant high or low inputs depending on their position.

The eight high-efficiency LEDs are anode-connected to the Zynq via 330 Ω resistors, so they will turn on when a logic high voltage is applied to their respective I/O pin. A schematic is given of the DSDB board on Canvas for those that are interested. Additional LEDs that are not user-accessible indicate power-on (PGOOD), FPGA programming status (DONE), and USB and Ethernet port status.

You should use the following items for your ports in your top-level module as shown in Table 1. You do not have to use all of the items, but they are there to use for inputs, outputs, or debugging. You should also test your design so it works for all 8 combinations of inputs.

3.1 How to get started?

To get you started there are a couple of downloads that will help you get started. All of these files are found within a zip file on Canvas called `lab0.zip`. The first item is a complete SV file, testbench and DO file you can use as a template for your test. Second, there is a zip file of a demo program. The demo program does not have anything in it except a blank SV file that you should modify. Feel free to modify the file name or module name, if you wish, as well.

The included complete `silly.sv` SV HDL file is just a sample Verilog file that implements a silly Boolean function (i.e., the same SV HDL file found in Chapter 4 of your textbook [1]). A DO or Tcl file is a script that simulates your design through ModelSim. To simulate your `silly.sv`, go to a terminal and type:

```
vsim -do silly.do
```

You should use these files, once you understand how to simulate something, to build the required Verilog file for this laboratory (i.e., the full adder circuit).

Once you design your SV of your full adder and test it thoroughly, implement it on the FPGA board. It is important that your design work in simulation **before** you even go to implementing on your FPGA board. This should be fairly easy if you use the demo program (i.e., zipped file) to insert your file into the

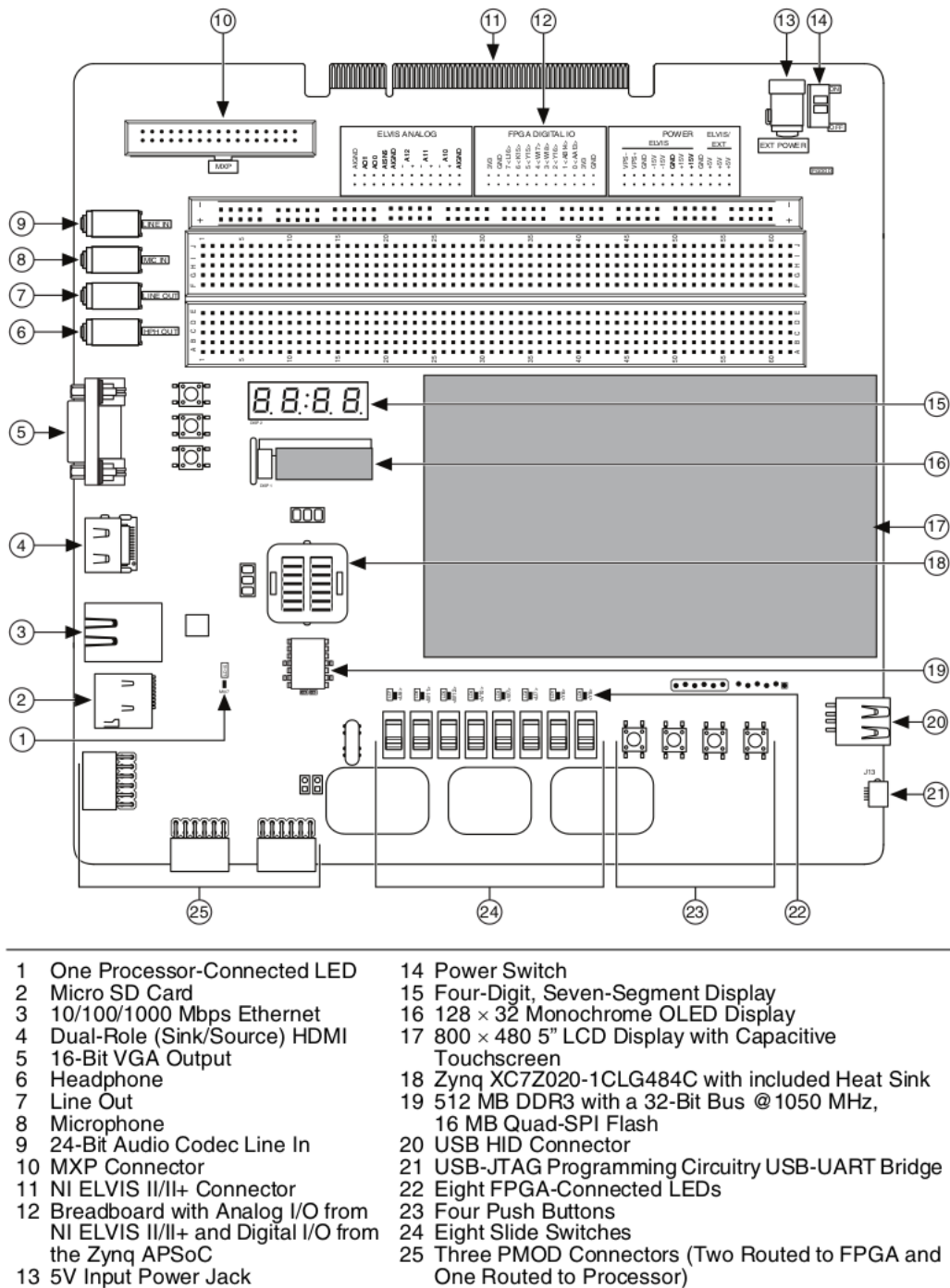
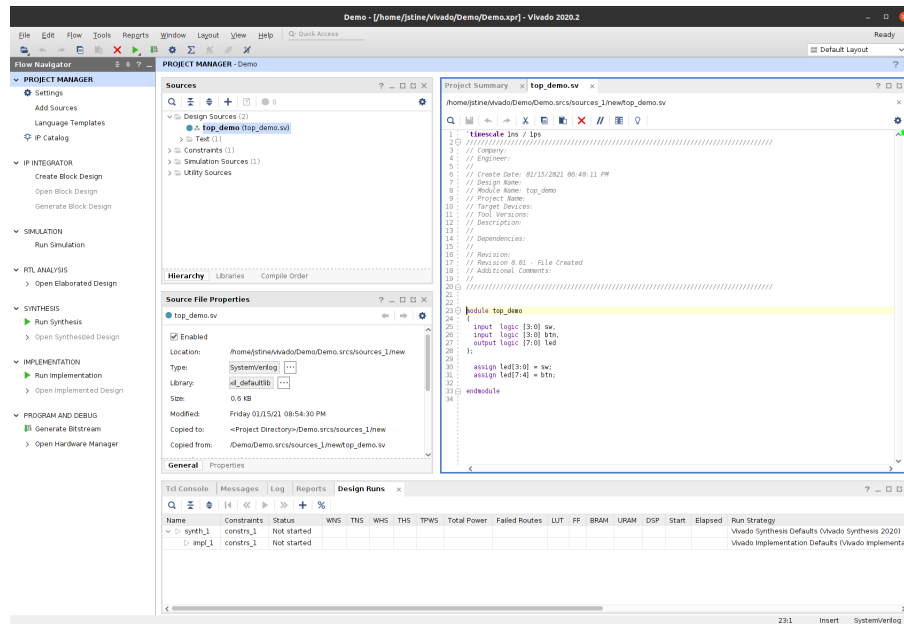


Figure 1: The NI Digital System Development Board [2]

Figure 2: The `top_demo` opened project inside Xilinx Vivado

design. That is, once inside Vivado, open the unzipped file by navigating through **File->Project->Open** and opening the `Demo.xpr` project. Once the project has opened, go to the `top_demo.vv` source by double-clicking the `top_demo` design. It should look like Figure 2 and you can now replace your ModelSim-tested HDL into the `top_demo` SV file. You can either copy your working HDL into the `top_demo` SV file or instantiate your full adder as discussed in class. Once inserted, then synthesize and implement your design. Synthesizing and implementing your design on the FPGA normally takes several minutes and so this is why we spend so much time designing our HDL before we get to this step.

The Xilinx Vivado software is very complex and its going to take a while to understand how to get more complicated designs through. For now, first make sure your SV completes the test correctly (i.e., through all 8 combinations in ModelSim). Then, when inside Vivado, click the following on the left-hand sidebar to start the process of implementing onto the FPGA.

1. Run Synthesis
2. Run Implementation
3. Generate Bitstream

This should take a little bit of time, but once complete, the design should be ready to download to the board.

To download to the board, click **Open Hardware Manager** on the left-hand sidebar and then you can either click **Program Device** on the left-hand sidebar or at the top of the screen. Once implemented, the device should be running. Then, use the LEDs and buttons to test your design to see if it works as your simulation did. You can also, if needed, print out a schematic of your design by clicking the **Schematic** option under the **RTL Analysis** section on the left-hand sidebar.

As we learned in class, combinations is a selection of items from a collection. You only have two options per input, which amounts to $2^3 = 8$ possible combinations of inputs. Make a table of all 8 possible input combinations and their respective output for the implementation using the LEDs to help debug what is going on. You should keep a record of this testing to make sure things worked as expected. The output should match the testing you saw in your ModelSim simulation. That is, you should test the 8 possible input combinations in ModelSim **and** in the implementation on the FPGA. Both versions of testing should match indicating your design worked as indicated.

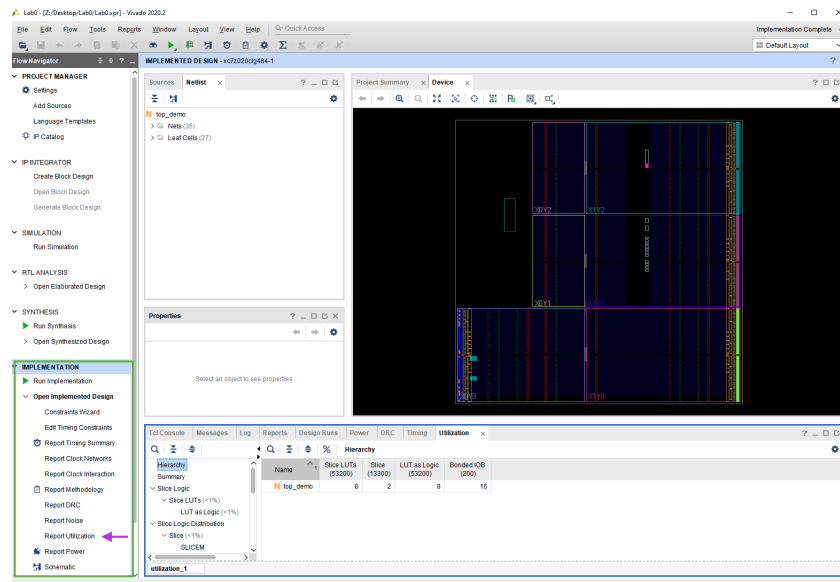


Figure 3: Implementation Window on Xilinx's Vivado

3.2 FPGA Implementation

You should also skim the document [3] and understand the differences between what an ASIC and a FPGA is. This document is also on Canvas, so you should download and read it lightly, paying special attention to Section II within the paper. Both ASICs and FPGAs are extremely similar in their structure, but can be different in terms of their implementation. However, they both use HDLs and using the methodology discussed in class benefits both implementations. Inside your lab report, you should indicate why FPGAs are important and how they can be utilized to implement digital gates efficiently.

3.2.1 Power, Performance and Area (PPA)

Digital systems typically employ outputs that indicate statistics of how much space and time is consumed on a device. These are typically allotted into an analysis called Power, Performance and Area (PPA) analysis. You should document in your report how much PPA is utilized for your final design.

During synthesis Vivado takes many of your HDL constructs and translates them to their implementation. As a designer, it is important to keep your design as similar as possible to what the digital logic represents. However, there is a good chance that your HDL usage may not look similar to the implemented design. This is because Xilinx Vivado as well as many other synthesis programs utilize High-Level Synthesis (HLS). Right now, only commercial tools truly support HLS, but there more synthesis programs in the future will support HLS. Fortunately, Xilinx Vivado truly supports HLS.

For future laboratories, we will explore the PPA of your design, but for this lab you should only report your final area for your final design. The area for the Xilinx FPGA is reported in “slices” utilized. You can find this information by “Open Implemented Design” on the left side of the screen and then clicking the “Report Utilization” tab, as seen in Figure 3. This should produce output that gives the total number of “slices” used for your design. Interestingly, you can also look at the Schematic it produces by clicking the Schematic option on the “Open Implemented Design” tab. For these laboratories, you should just report the total “Slices” for your LUTs which you can find in the Summary part of the Utilization Report. LUTs are the look-up tables discussed in [3].

4. Handin

You should electronically hand in your HDL (all files that you want us to see) into Canvas. You should also take a printout of your waveform from your ModelSim simulation. Only one of your team members should

upload the files and/or lab report. Although we only need one lab report, each team member should upload their team assessment form. You can upload them together or separately; to get credit for the laboratory, we must receive this team assessment. Please contact the James Stine (james.stine@okstate.edu) for more help. Your code should be readable and well-documented. In addition, please turn in additional test cases or any other added item that you used. Please also remember to document everything in your Lab Report using the information found in the Grading Rubric.

References

- [1] S. Harris and D. Harris, *Digital Design and Computer Architecture: RISC-V Edition*, 1st ed. San Francisco, CA, USA: Morgan Kaufmann Publishers Inc., 2021.
- [2] “User Manual: NI Digital System Development Board,” National Instruments, Tech. Rep. Pub ID: 376627B-01, 2018.
- [3] S. M. Trimberger, “Three ages of FPGAs: A retrospective on the first thirty years of FPGA technology,” *Proceedings of the IEEE*, vol. 103, no. 3, pp. 318–331, 2015.